Jameco Part number 134914

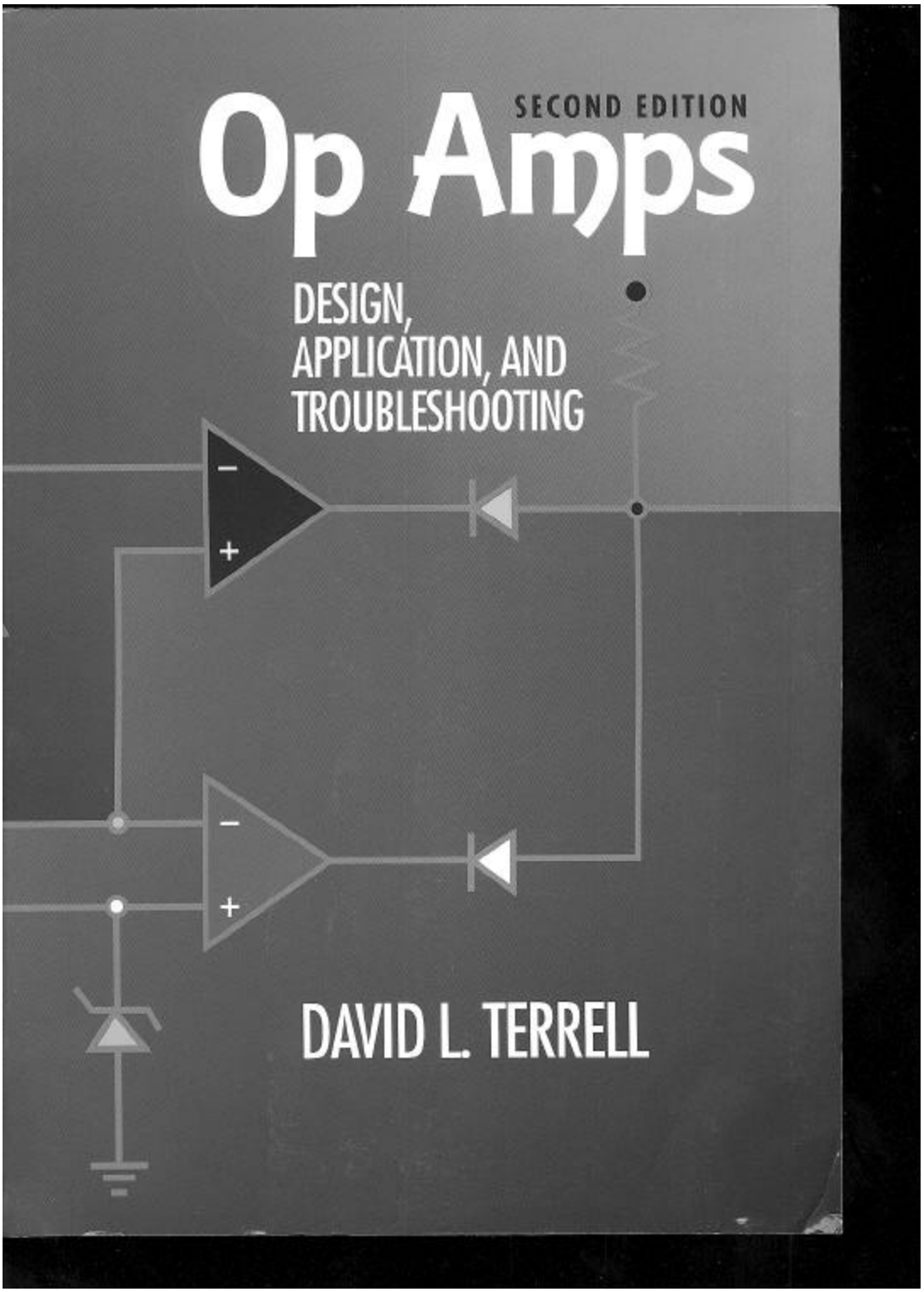

Jameco Part number 134914

CONTENTS

Preface *xi*

1 BASIC CONCEPTS OF THE INTEGRATED OPERATIONAL AMPLIFIER **1**

1.1 Overview of Operational Amplifiers 1
1.2 Review of Important Basic Concepts 5
1.3 Basic Characteristics of Ideal Op Amps 13
1.4 Introduction to Practical Op Amps 18
1.5 Circuit Construction Requirements 25
1.6 Electrostatic Discharge 31

2 AMPLIFIERS **36**

2.1 Amplifier Fundamentals 36
2.2 Inverting Amplifier 39
2.3 Noninverting Amplifier 58
2.4 Voltage Follower 72
2.5 Inverting Summing Amplifier 78
2.6 Noninverting Summing Amplifier 93
2.7 AC-Coupled Amplifier 95
2.8 Current Amplifier 111
2.9 High-Current Amplifier 118
2.10 Troubleshooting Tips for Amplifier Circuits 130

3 VOLTAGE COMPARATORS **134**

3.1 Voltage Comparator Fundamentals 134
3.2 Zero-Crossing Detector 135

3.3 Zero-Crossing Detector with Hysteresis 141
3.4 Voltage Comparator with Hysteresis 149
3.5 Window Voltage Comparator 156
3.6 Voltage Comparator with Output Limiting 161
3.7 Troubleshooting Tips for Voltage Comparators 170
3.8 Nonideal Considerations 171

4 OSCILLATORS 173

4.1 Oscillator Fundamentals 173
4.2 Wien-Bridge Oscillator 174
4.3 Voltage-Controlled Oscillator 180
4.4 Variable-Duty Cycle 190
4.5 Triangle-Wave Oscillator 204
4.6 Troubleshooting Tips for Oscillator Circuits 209
4.7 Nonideal Considerations 210

5 ACTIVE FILTERS 212

5.1 Filter Fundamentals 212
5.2 Low-Pass Filter 214
5.3 High-Pass Filter 221
5.4 Bandpass Filter 228
5.5 Band Reject Filter 236
5.6 Troubleshooting Tips for Active Filters 246

6 POWER SUPPLY CIRCUITS 248

6.1 Voltage Regulation Fundamentals 248
6.2 Series Voltage Regulators 256
6.3 Shunt Voltage Regulation 265
6.4 Switching Voltage Regulators 275
6.5 Over-Current Protection 279
6.6 Over-Voltage Protection 282
6.7 Power-Fail Sensing 285
6.8 Troubleshooting Tips for Power Supply Circuits 286

7 SIGNAL PROCESSING CIRCUITS 289

7.1 The Ideal Diode 289
7.2 Ideal Rectifier Circuits 291
7.3 Ideal Biased Clipper 299
7.4 Ideal Clamper 307
7.5 Peak Detectors 316

Jameco Part number 134914

7.6 Integrator 323
7.7 Differentiator 330
7.8 Troubleshooting Tips for Signal Processing Circuits 336

8 DIGITAL-TO-ANALOG AND ANALOG-TO-DIGITAL CONVERSION **337**
8.1 D/A and A/D Conversion Fundamentals 338
8.2 Weighted D/A Converter 344
8.3 R2R Ladder D/A Converter 347
8.4 Parallel A/D Converter 349
8.5 Tracking A/D Converter 351
8.6 Dual-Slope A/D Converter 353
8.7 Successive Approximation A/D Converter 357

9 ARITHMETIC FUNCTION CIRCUITS **360**
9.1 Adder 360
9.2 Subtractor 366
9.3 Averaging Amplifier 370
9.4 Absolute Value Circuit 371
9.5 Sign Changing Circuit 377
9.6 Troubleshooting Tips for Arithmetic Circuits 380

10 NONIDEAL OP AMP CHARACTERISTICS **383**
10.1 Nonideal DC Characteristics 383
10.2 Nonideal AC Characteristics 392
10.3 Summary and Recommendations 401

11 SPECIALIZED DEVICES **404**
11.1 Programmable Op Amps 404
11.2 Instrumentation Amplifiers 405
11.3 Logarithmic Amplifiers 409
11.4 Antilogarithmic Amplifiers 411
11.5 Multipliers/Dividers 413
11.6 Single-Supply Amplifiers 416
11.7 Multiple Op Amp Packages 422
11.8 Hybrid Operational Amplifiers 422
Appendices *424*
Index *477*

Jameco Part number 134914

Electronics

Op Amps

DESIGN, APPLICATION, AND TROUBLESHOOTING

SECOND EDITION

DAVID L. TERRELL

Op Amps: Design, Application, and Troubleshooting, Second Edition straddles the imaginary line between the technician and engineering worlds. Topics are carefully addressed on three distinct levels:

Operational overview
Describes the purpose and explains the operation of each op amp circuit from an intuitive and non-mathematic viewpoint, including functional descriptions, purpose of components, circuit waveforms, and so forth.

Numerical analysis
Shows how to calculate important circuit parameters such as ac and dc voltages, amplification, frequency response, switching speeds, input and output impedances, and a host of other circuit values for a variety of op amp circuits.

Design techniques
Presents step-by-step design techniques for a wide range of op amp circuits, including basic amplifiers, comparators, oscillators, active filters, arithmetic circuits, signal processing circuits, and many others.

Troubleshooting techniques are presented that rely on the application of fundamental electronics principles. Systematic methods are shown that can be used to diagnose defects in many kinds of circuits that employ operational amplifiers.

Op Amps: Design, Application, and Troubleshooting, Second Edition explains the technical details of operational amplifier circuits in clear and understandable language without sacrificing technical depth.

David L. Terrell has over 20 years of experience as an educator, engineer, and technician in many phases of electronics, including fundamental electronics, solid-state devices, operational amplifiers, digital electronics, microprocessor technology, industrial control systems, ultrasonic detection systems, and aircraft electronics. He is the president of Terrell Technologies, Inc., a Florida-based firm specializing in the development of educational products and computer software.

BUTTERWORTH HEINEMANN

ISBN 0-7506-9702-4

90000

9 780750 697026